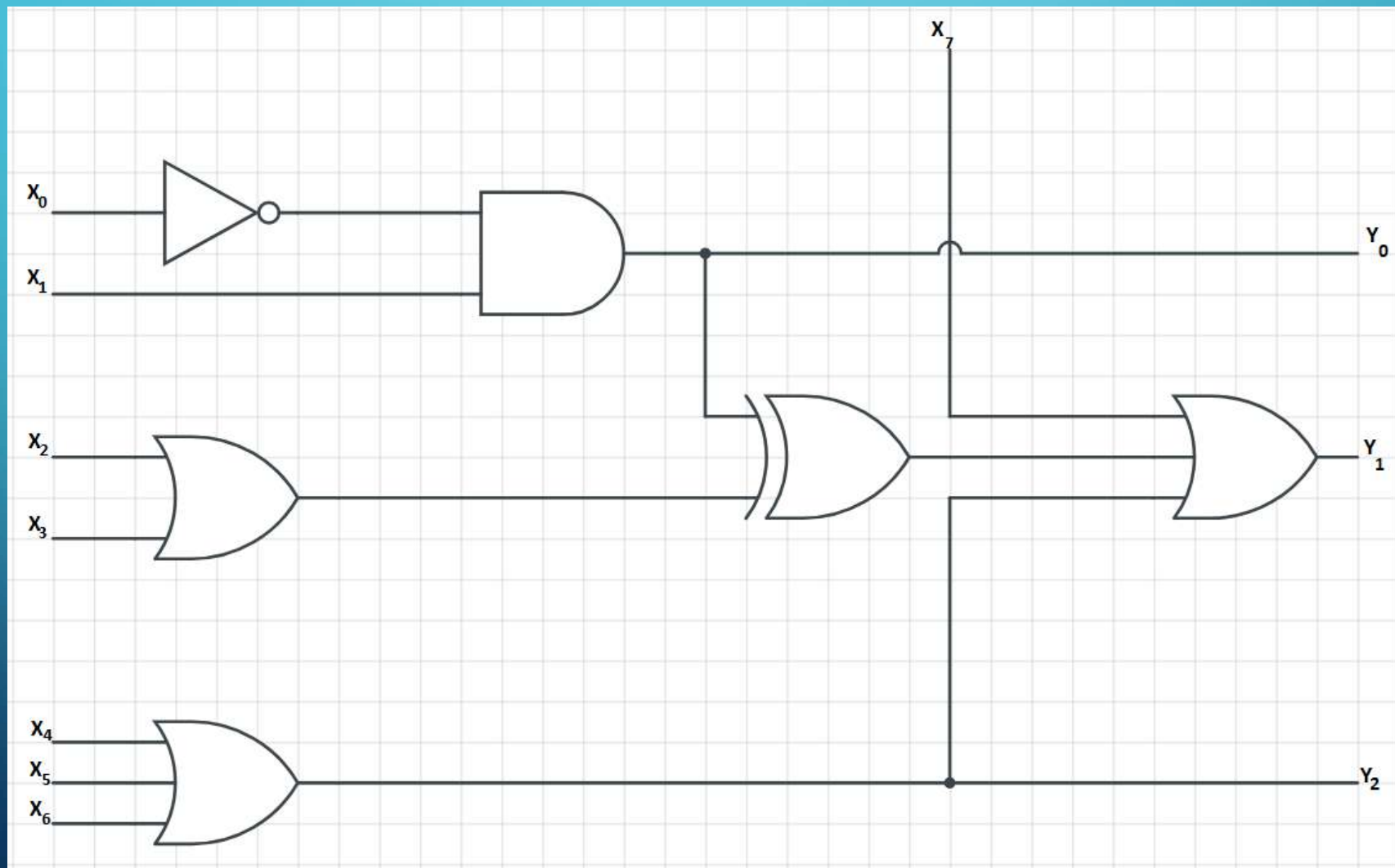


A decorative graphic on the left side of the slide, consisting of a network of light blue lines and small circles, resembling a circuit board or a neural network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are placed at various points along these lines.


COS 284 TUTORIAL 3

CLASS TEST 2 RECAP


FOR DECIMAL INPUT $X = 55$ WHAT IS THE OUTPUT?



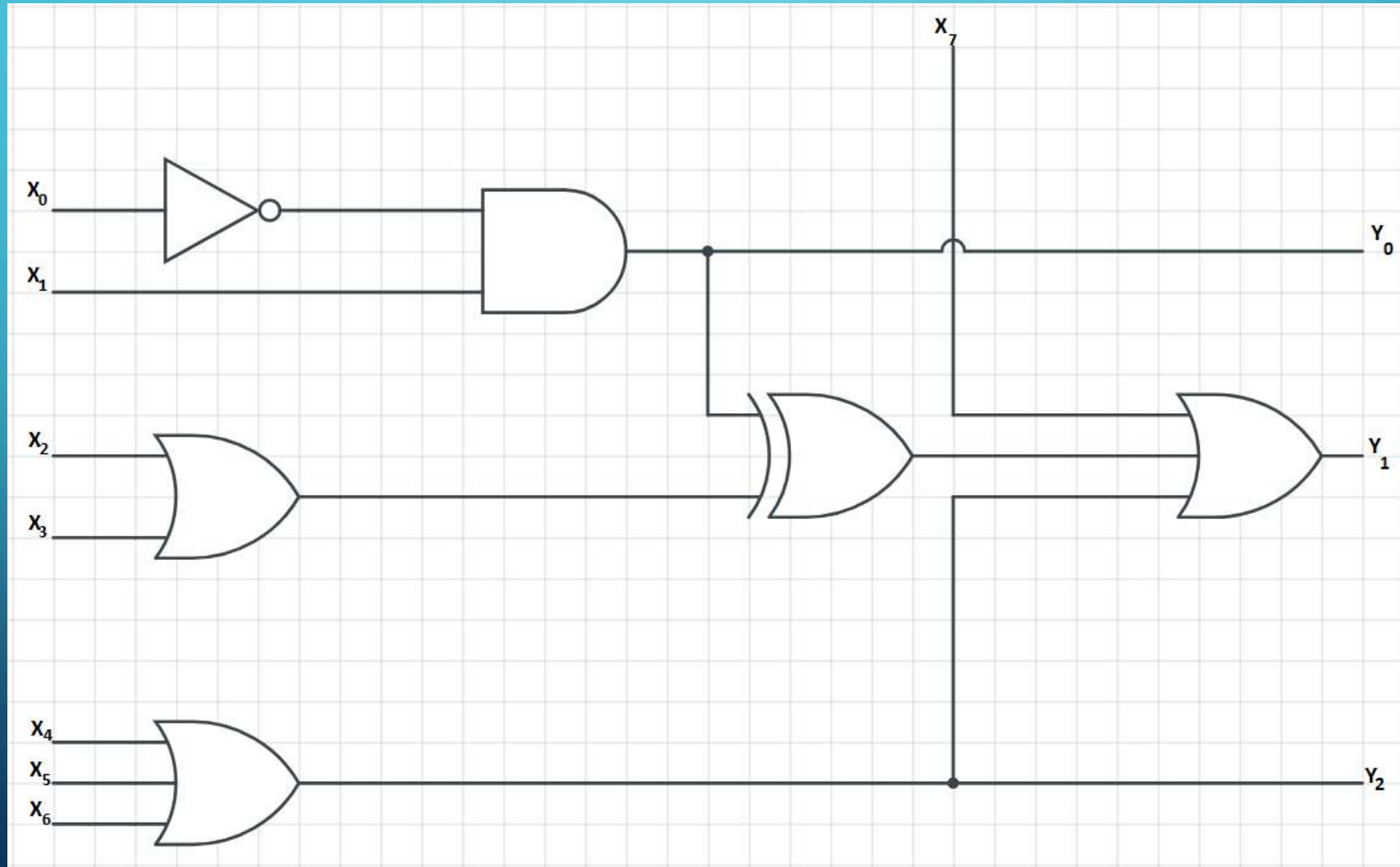
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



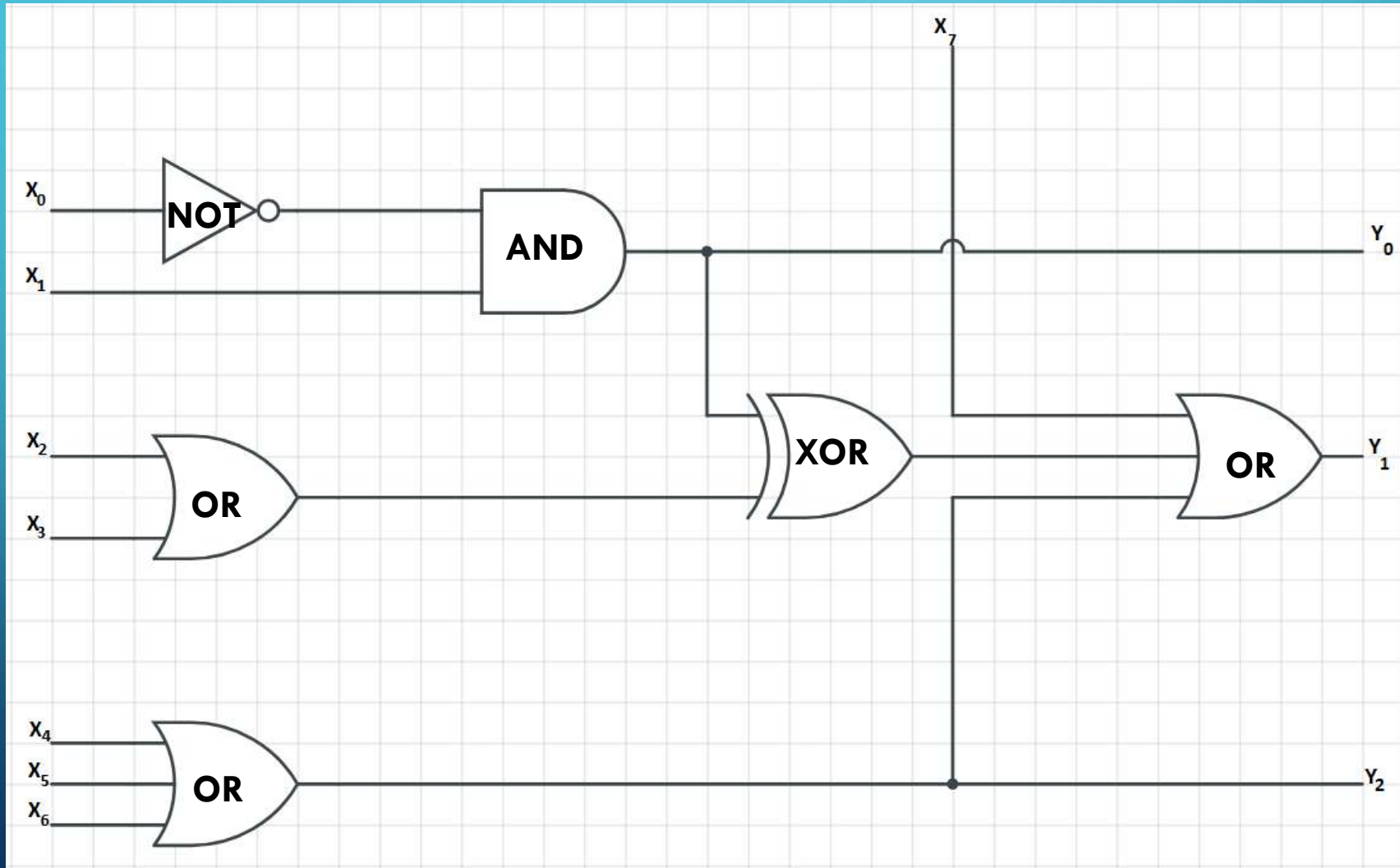
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



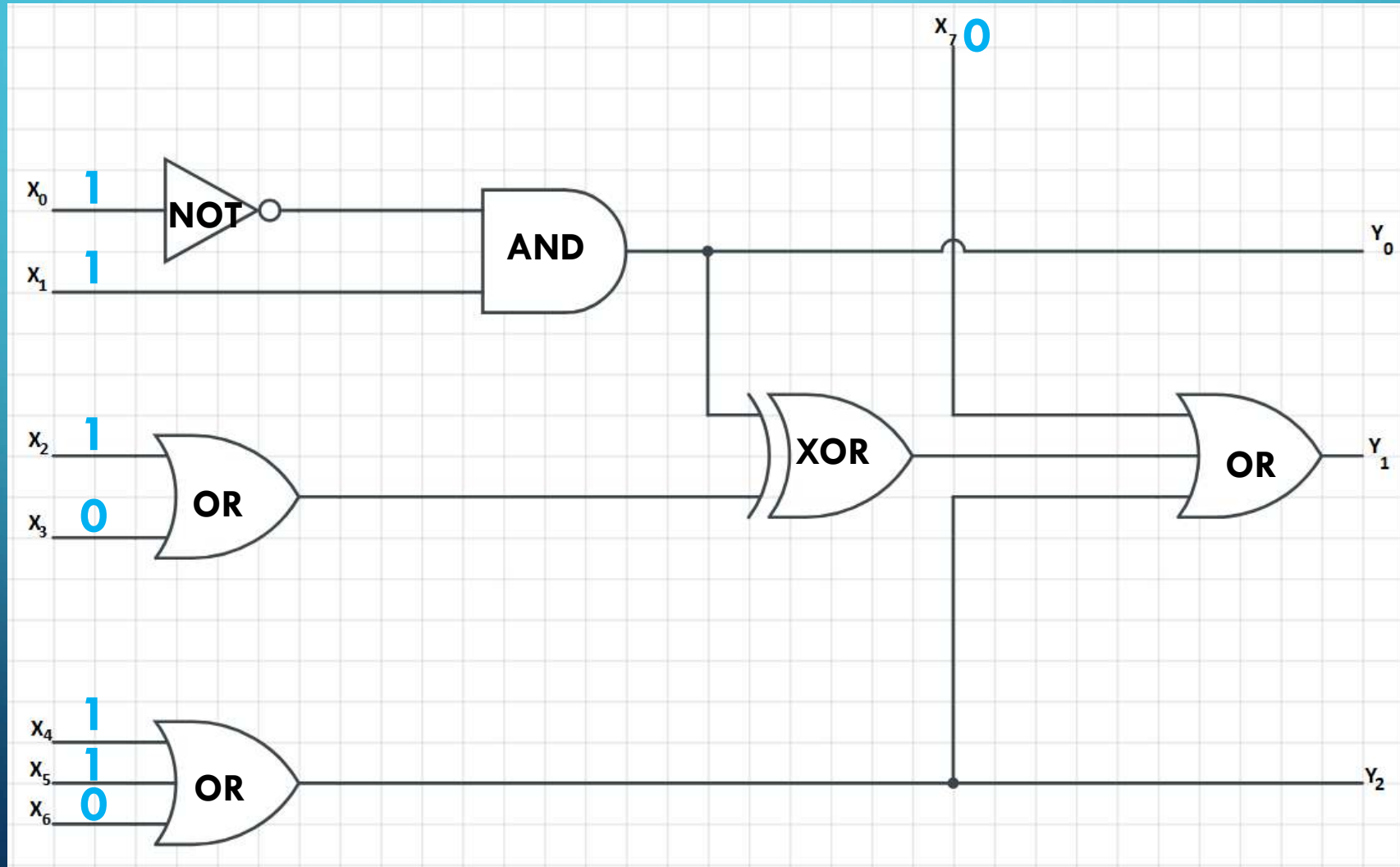
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



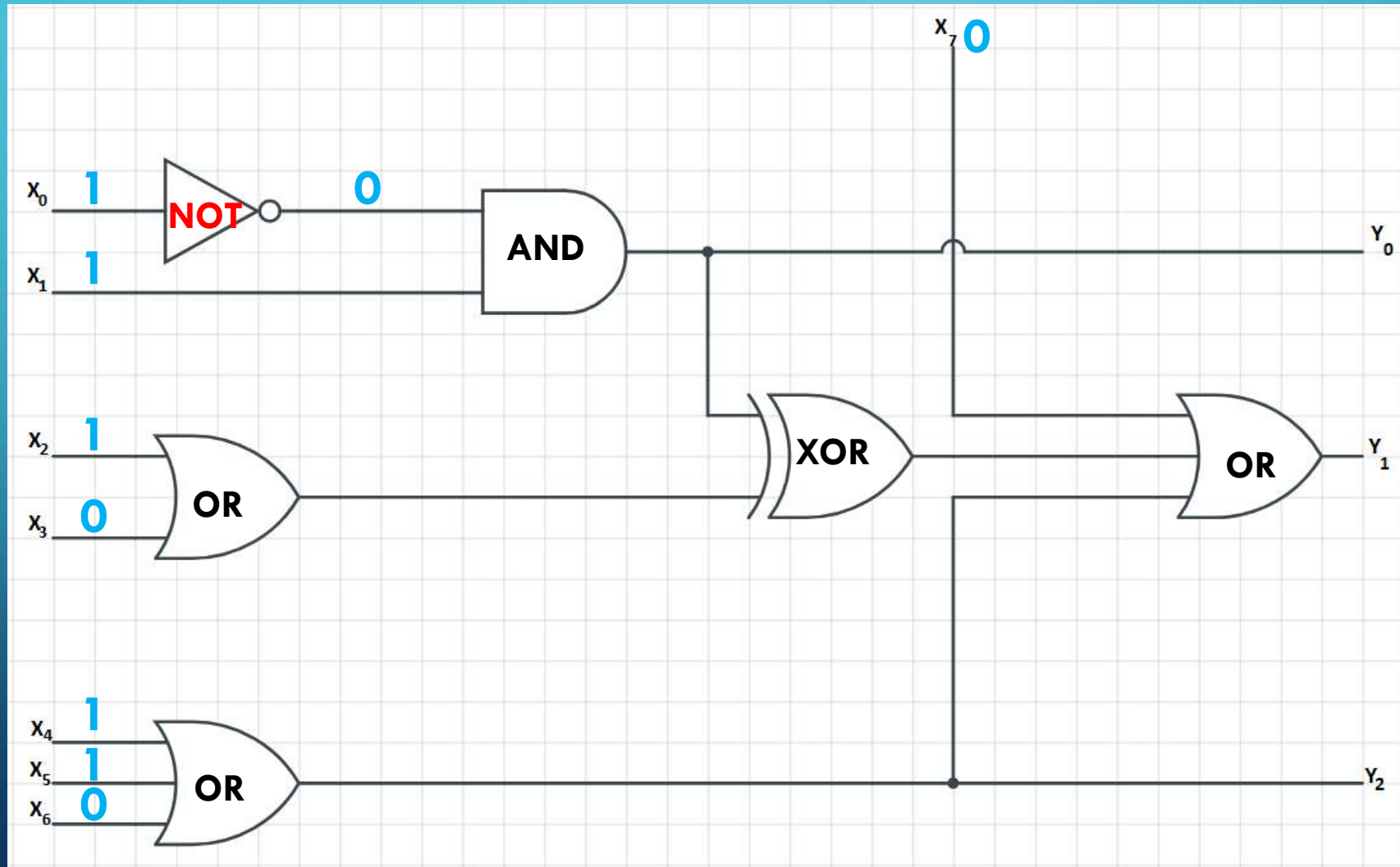
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



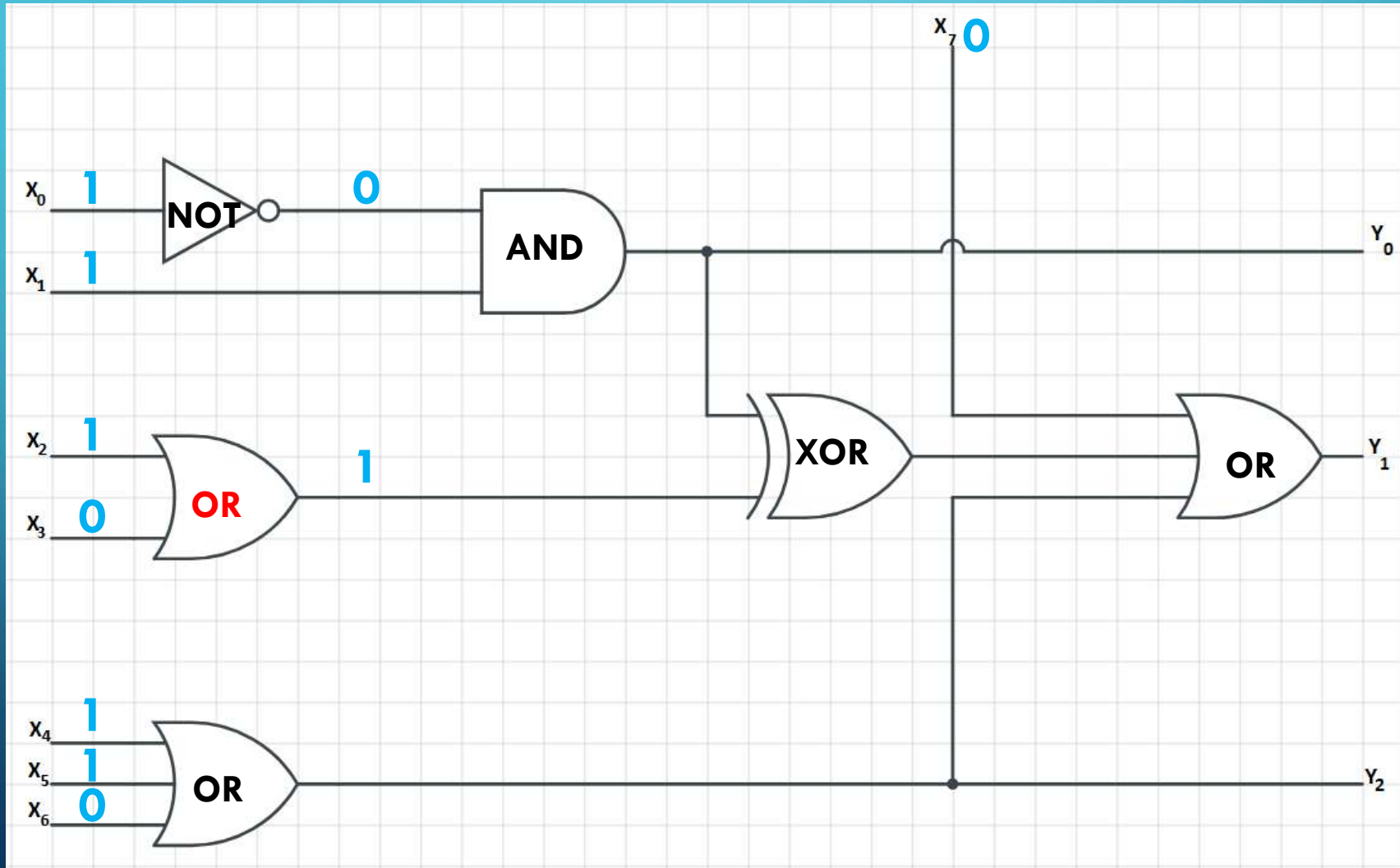
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



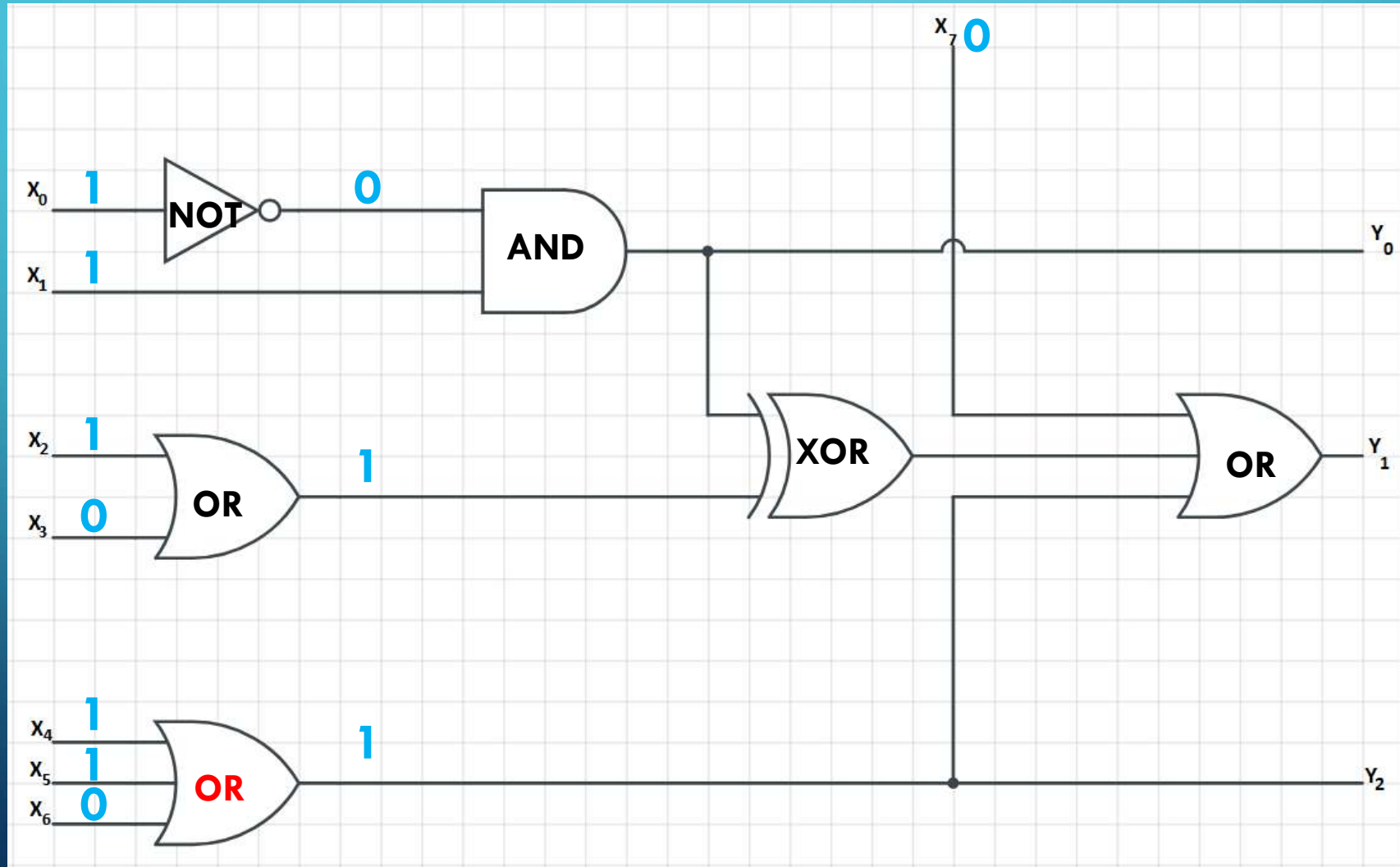
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



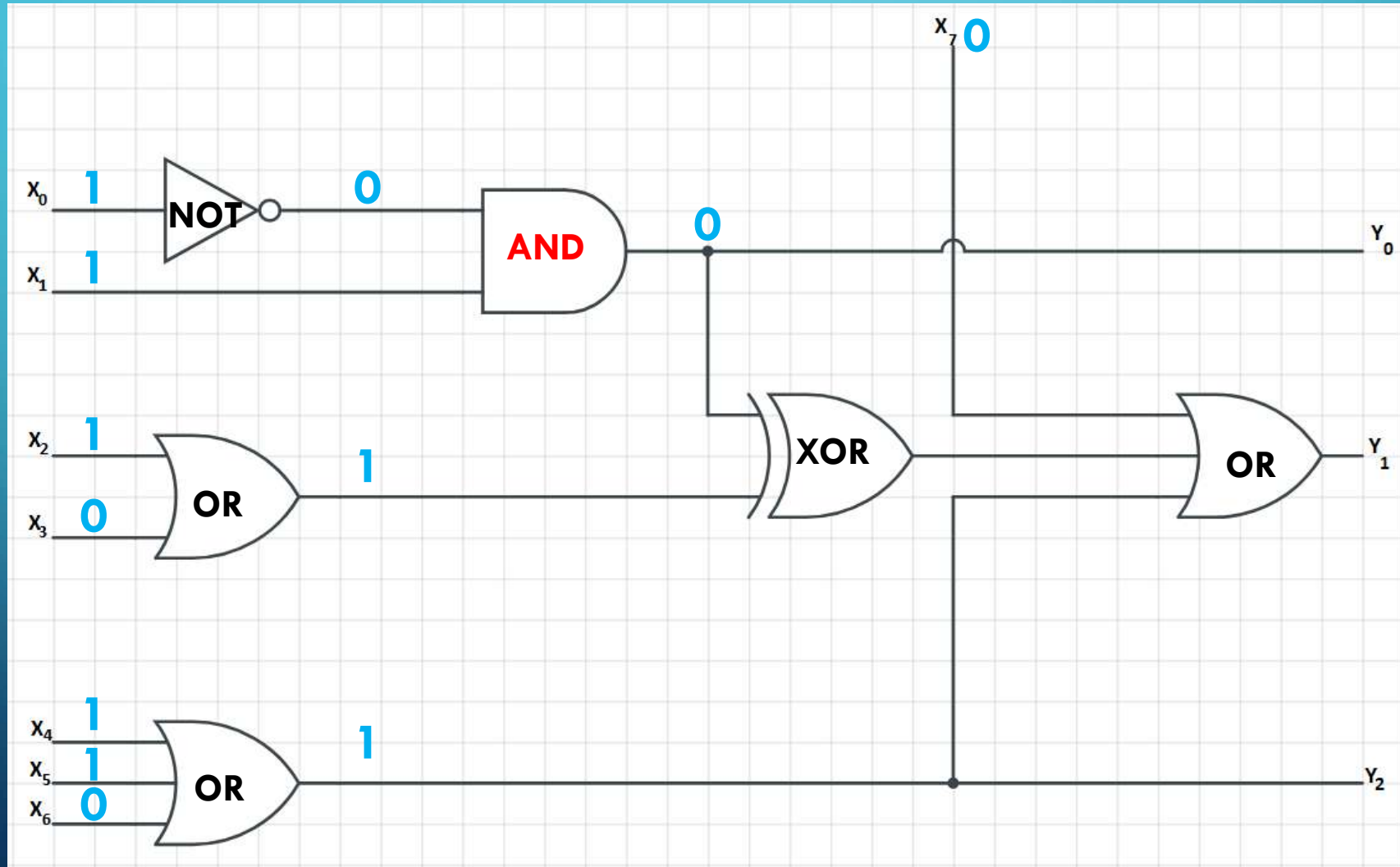
FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



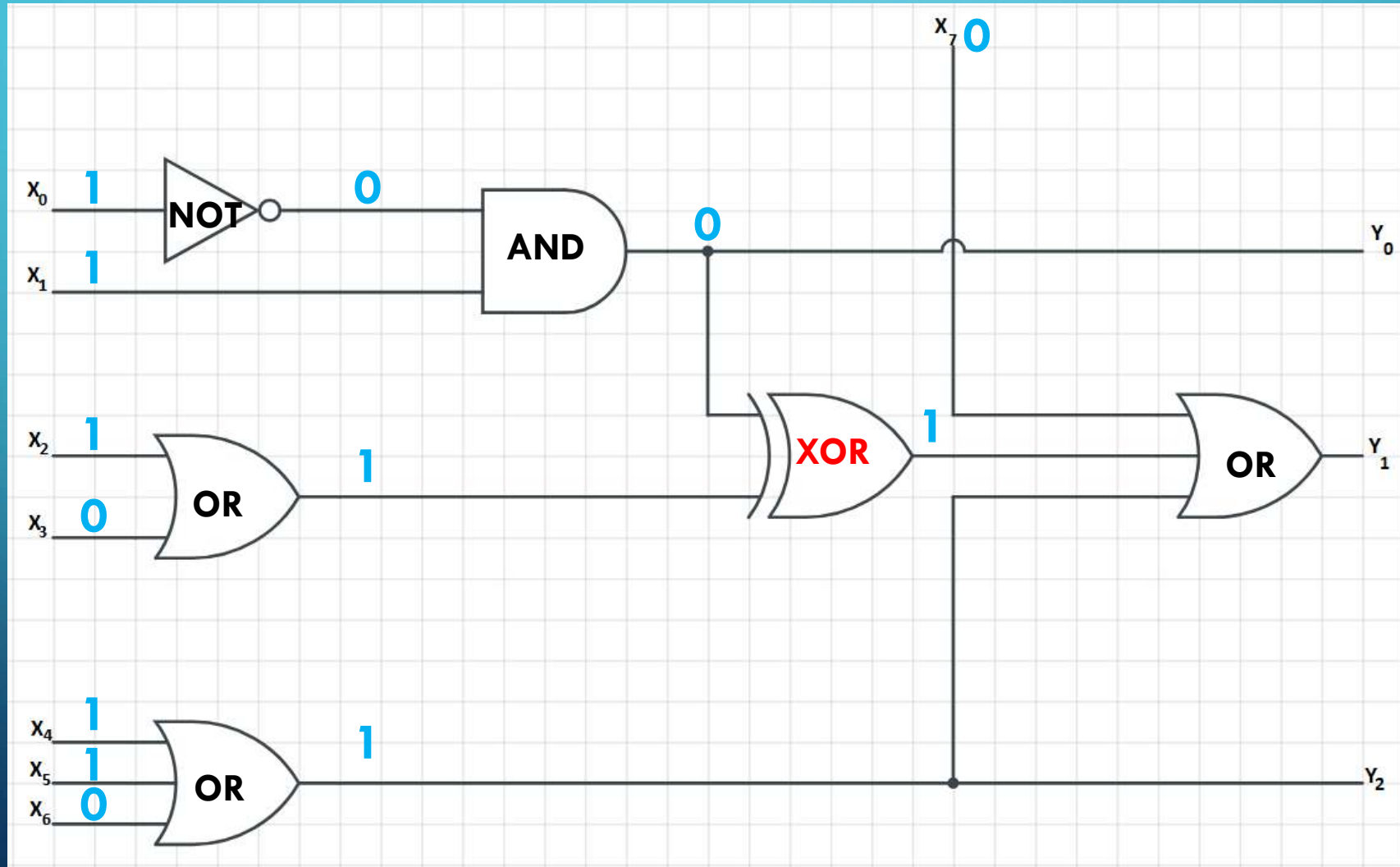FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?



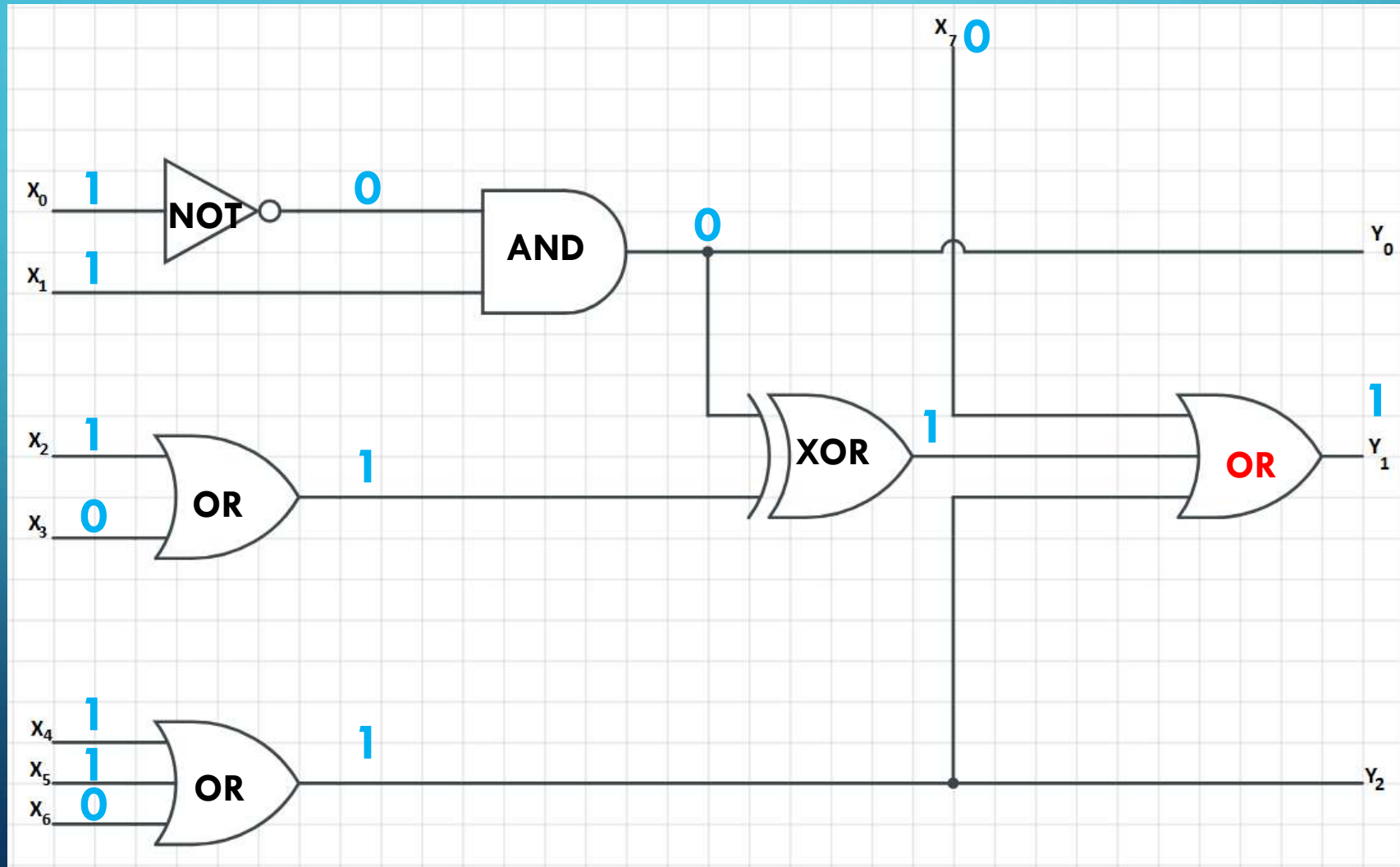FOR BINARY INPUT $x_7x_6x_5x_4x_3x_2x_1x_0 = 00110111$
WHAT IS THE OUTPUT?





DRAW A COMBINATIONAL CIRCUIT THAT
IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$


DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR NOT}(x \text{ AND } z) \text{ AND NOT}(y)$$


NOT operator has highest priority, followed by AND and then OR

DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR NOT}(x \text{ AND } z) \text{ AND NOT}(y)$$

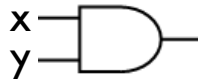NOT operator has highest priority, followed by AND and then OR





DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR NOT}(x \text{ AND } z) \text{ AND NOT}(y)$$

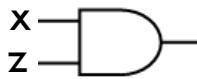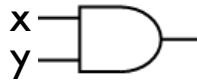NOT operator has highest priority, followed by AND and then OR






DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR } \text{NOT}(x \text{ AND } z) \text{ AND } \text{NOT}(y)$$

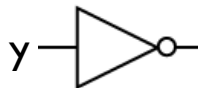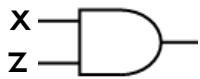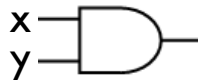NOT operator has highest priority, followed by AND and then OR






DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR } \text{NOT}(x \text{ AND } z) \text{ AND NOT}(y)$$

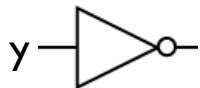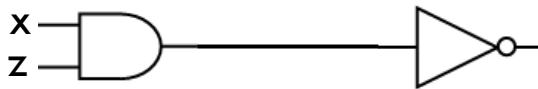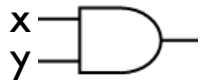NOT operator has highest priority, followed by AND and then OR




DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR } \text{NOT}(x \text{ AND } z) \text{ AND NOT}(y)$$

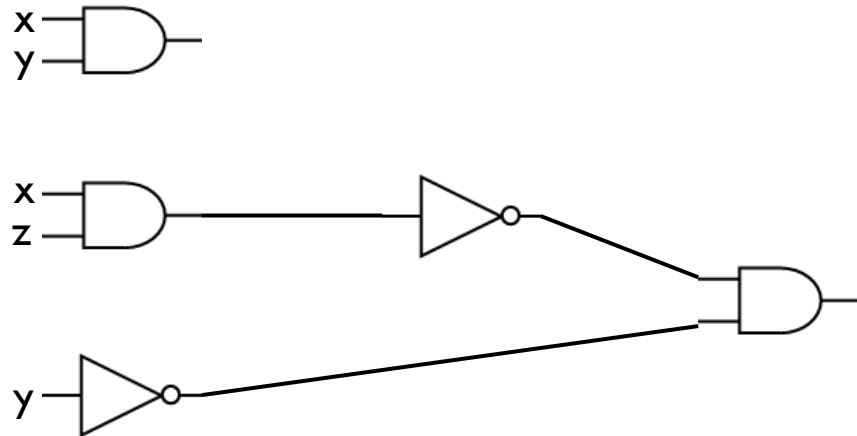NOT operator has highest priority, followed by AND and then OR




DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION

$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR } \text{NOT}(x \text{ AND } z) \text{ AND } \text{NOT}(y)$$

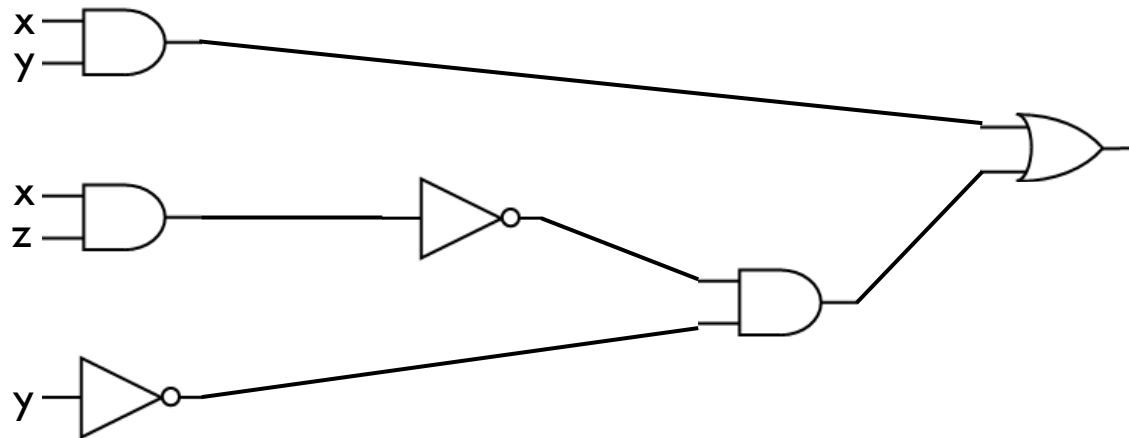NOT operator has highest priority, followed by AND and then OR




DRAW A COMBINATIONAL CIRCUIT THAT IMPLEMENTS THE GIVEN FUNCTION


$$F(x,y,z) = (xy) + (xz)'y'$$

$$= (x \text{ AND } y) \text{ OR } \text{NOT}(x \text{ AND } z) \text{ AND } \text{NOT}(y)$$

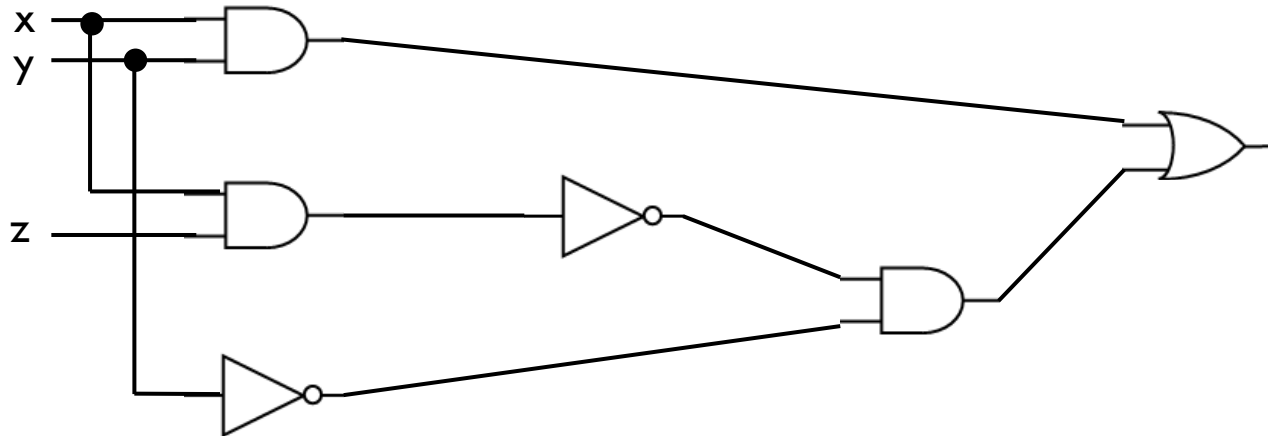
NOT operator has highest priority, followed by AND and then OR



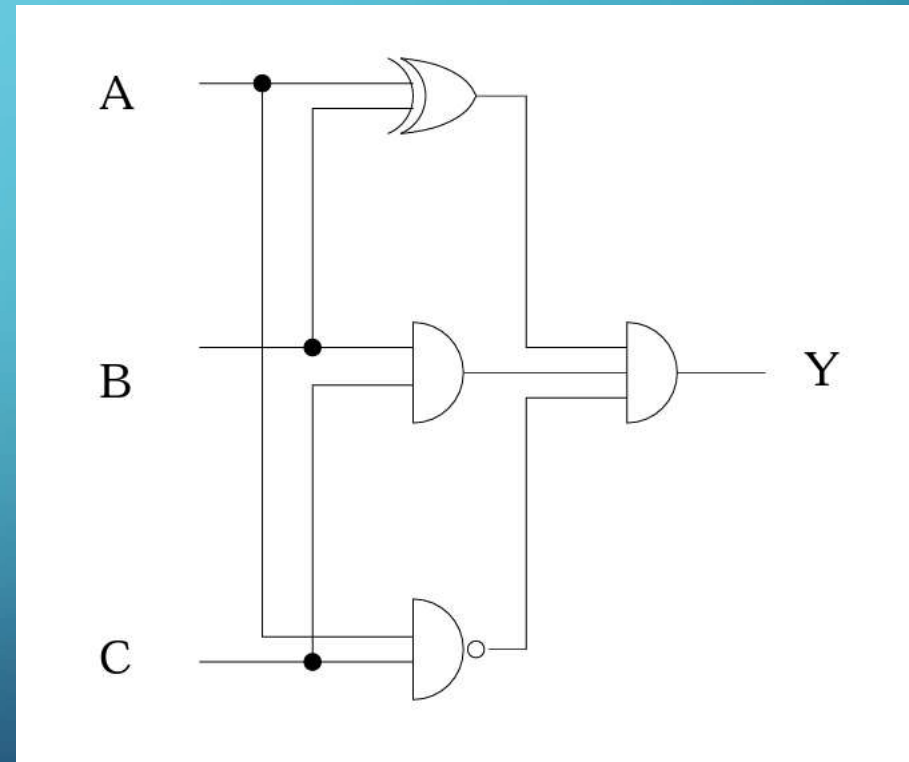PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT




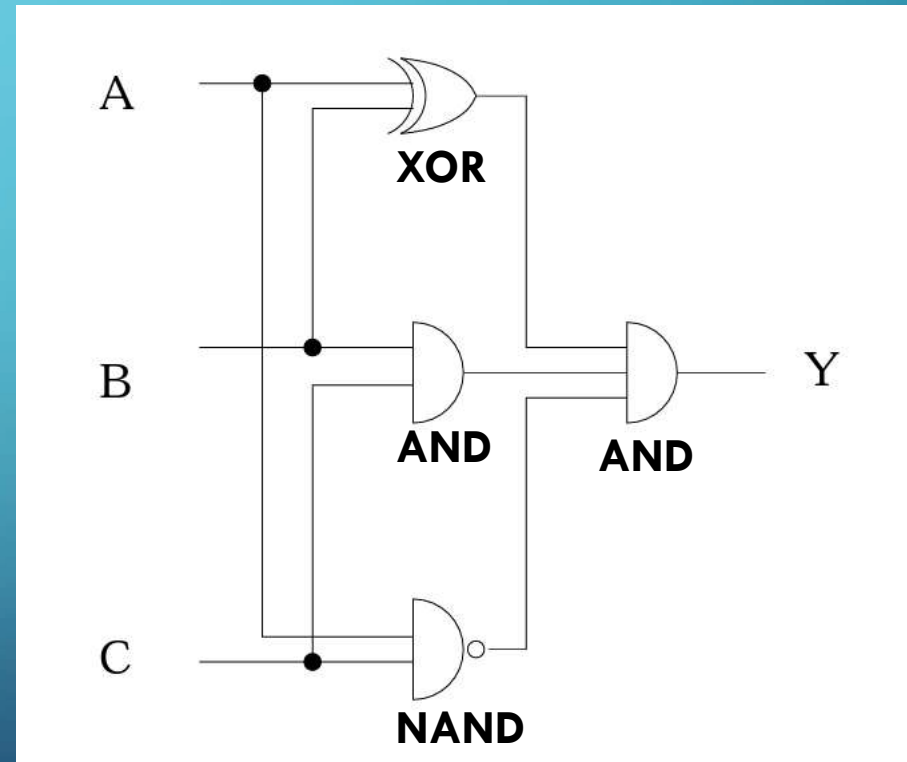PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT




PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

(A XOR B)

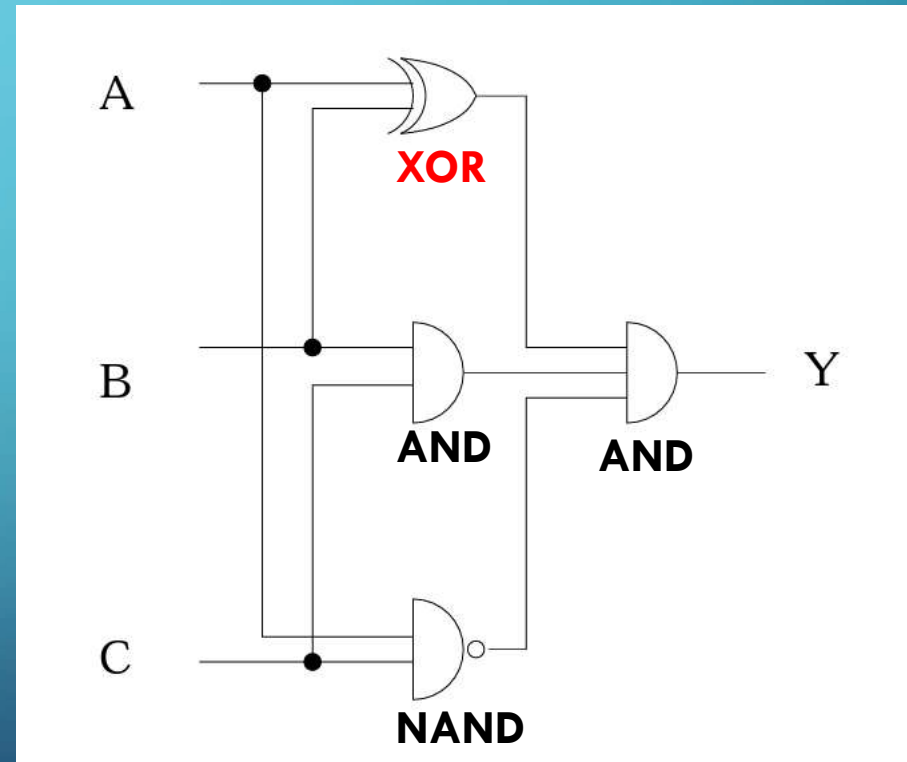


PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB'$$

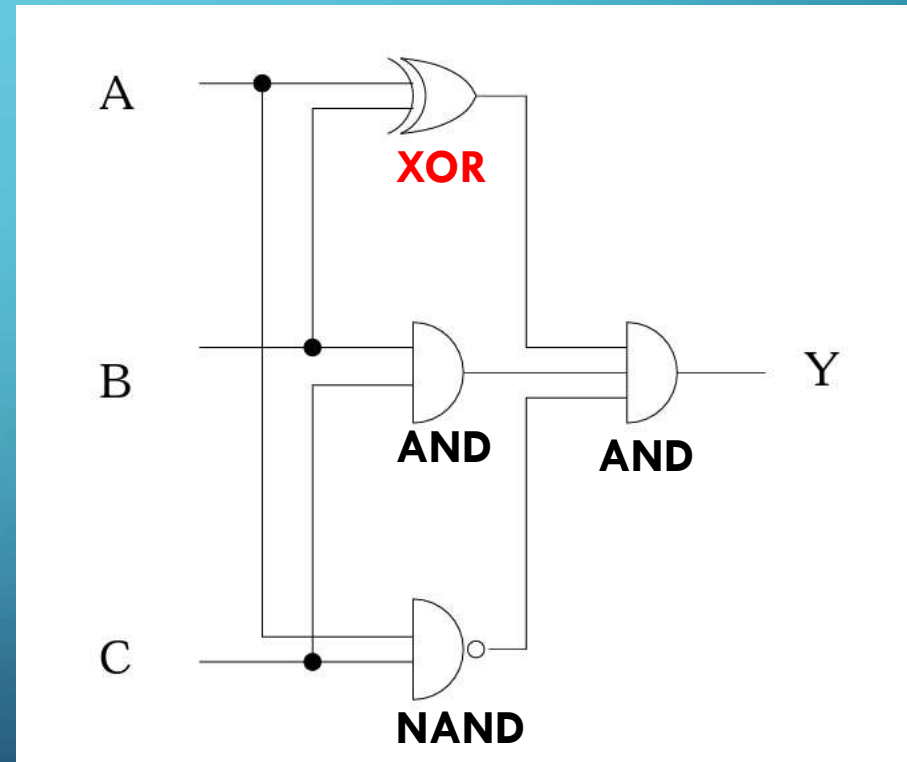

PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

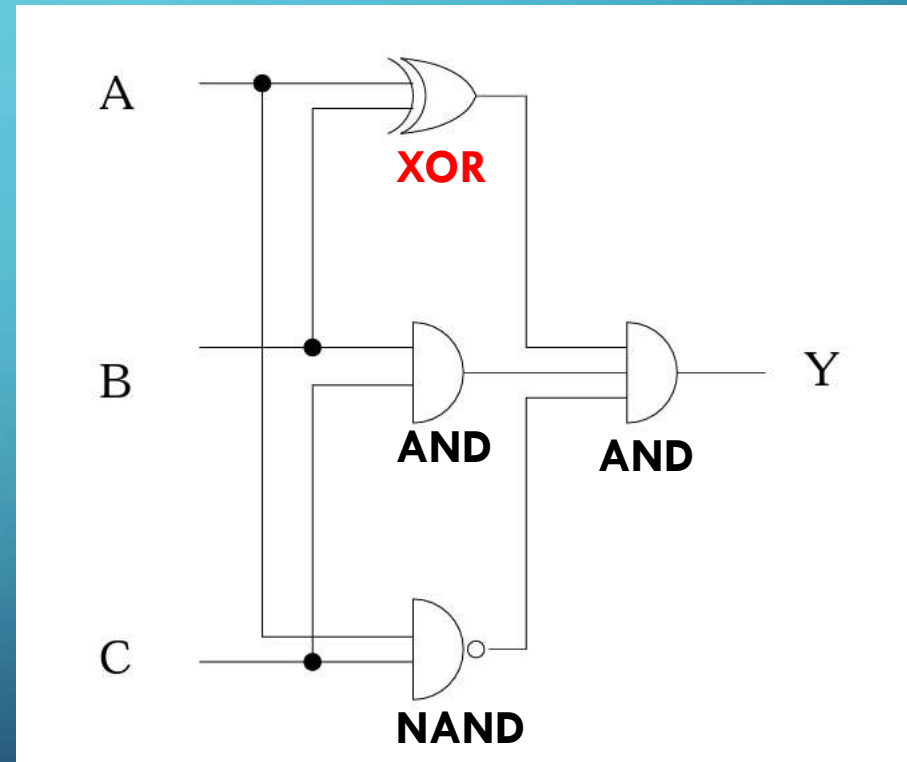
$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$



PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$


(B AND C)

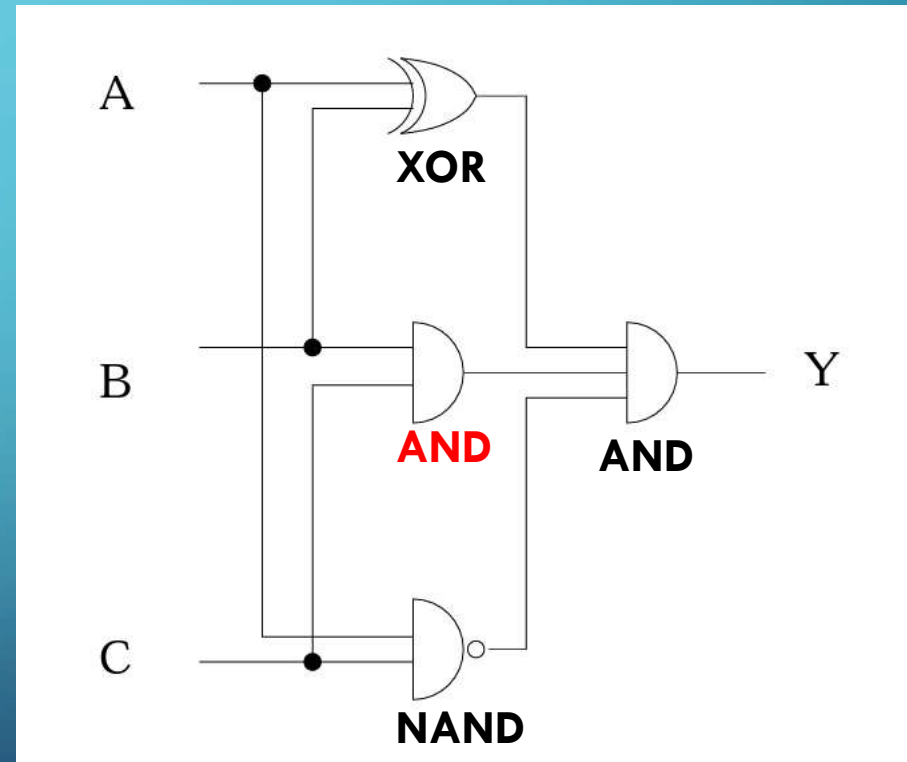

PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$


$$(B \text{ AND } C) = BC$$

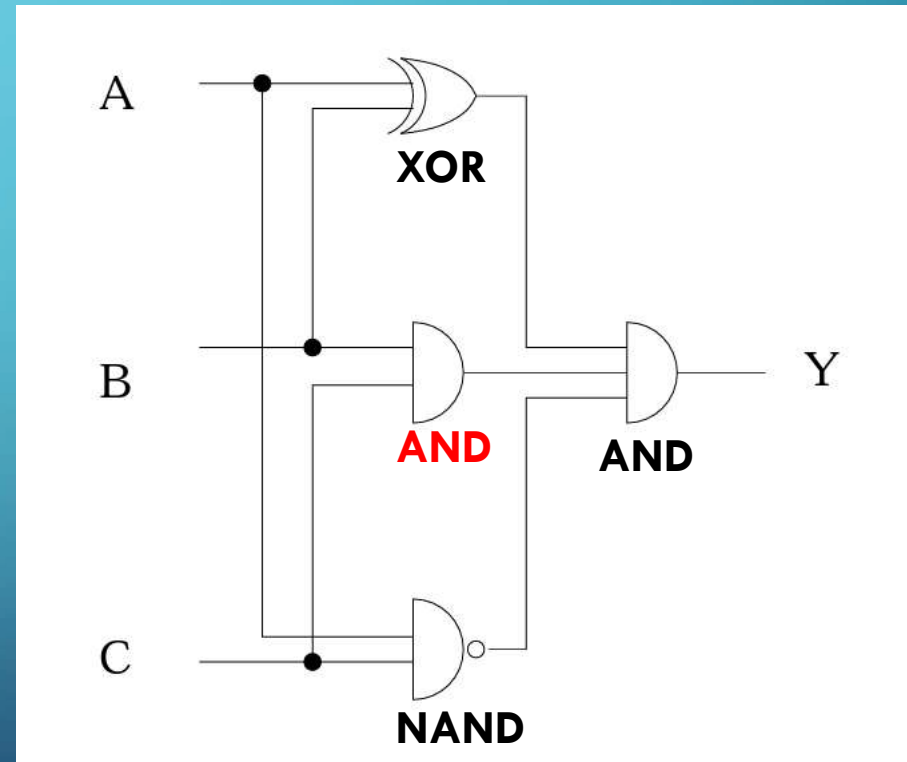

PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$

$$(B \text{ AND } C) = BC = (B)(C)$$

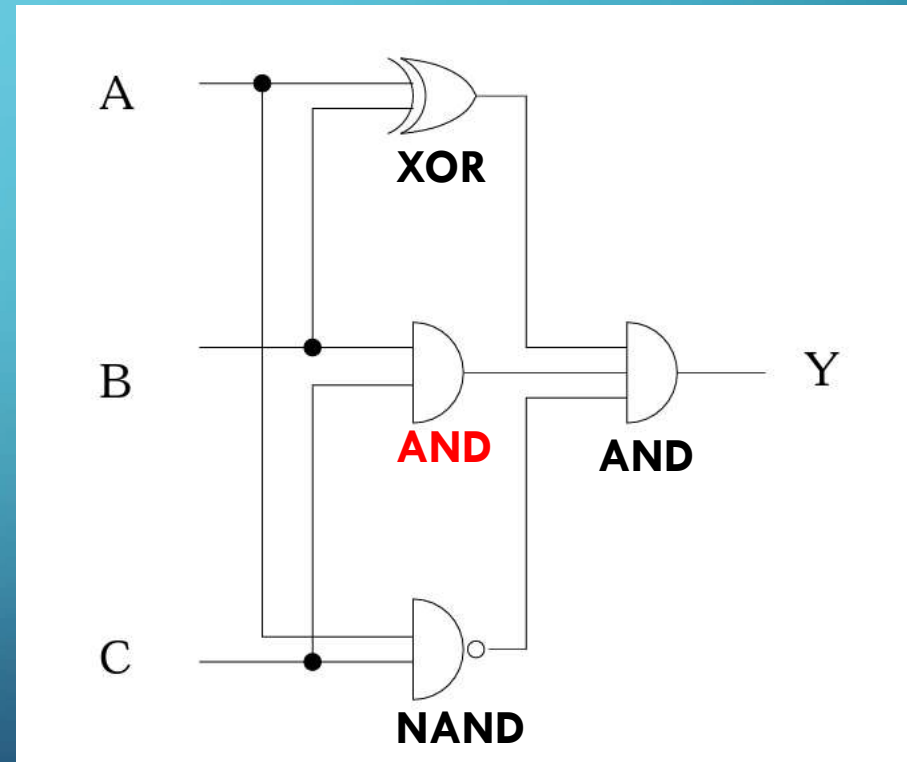


PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT
IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$

$$(B \text{ AND } C) = BC = (B)(C)$$

$$(A \text{ NAND } C)$$

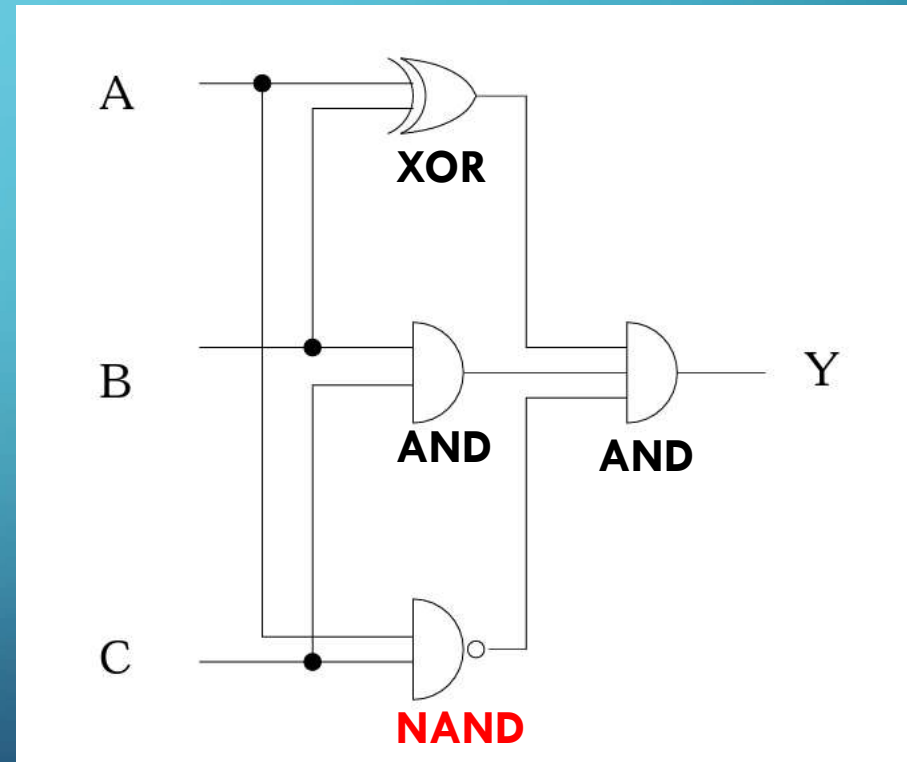


PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$

$$(B \text{ AND } C) = BC = (B)(C)$$

$$(A \text{ NAND } C) = (AC)'$$

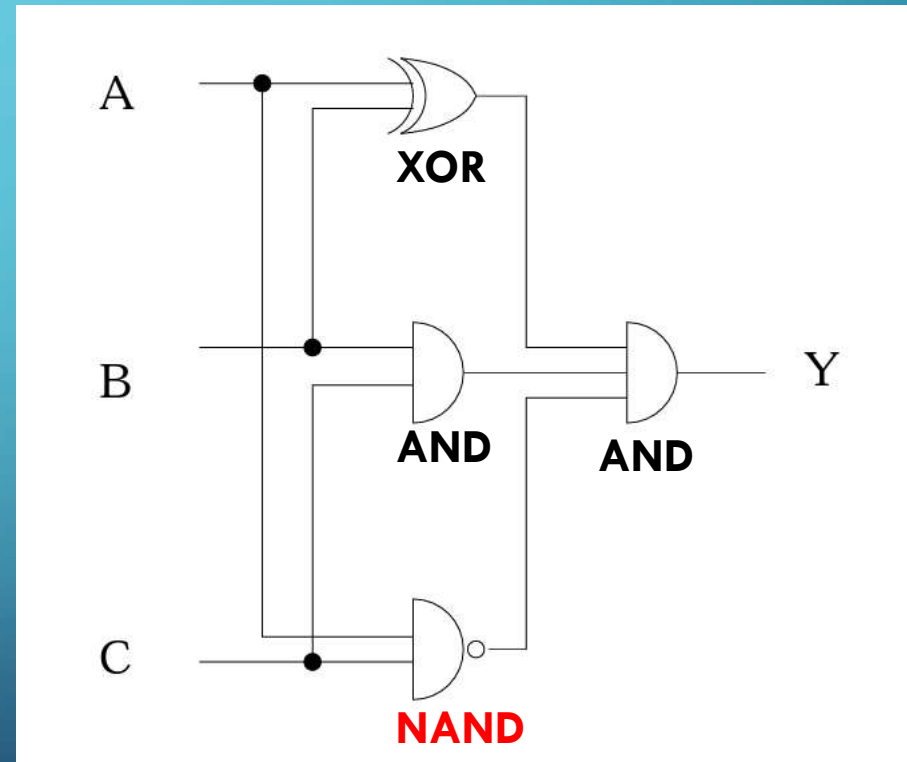


PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$

$$(B \text{ AND } C) = BC = (B)(C)$$
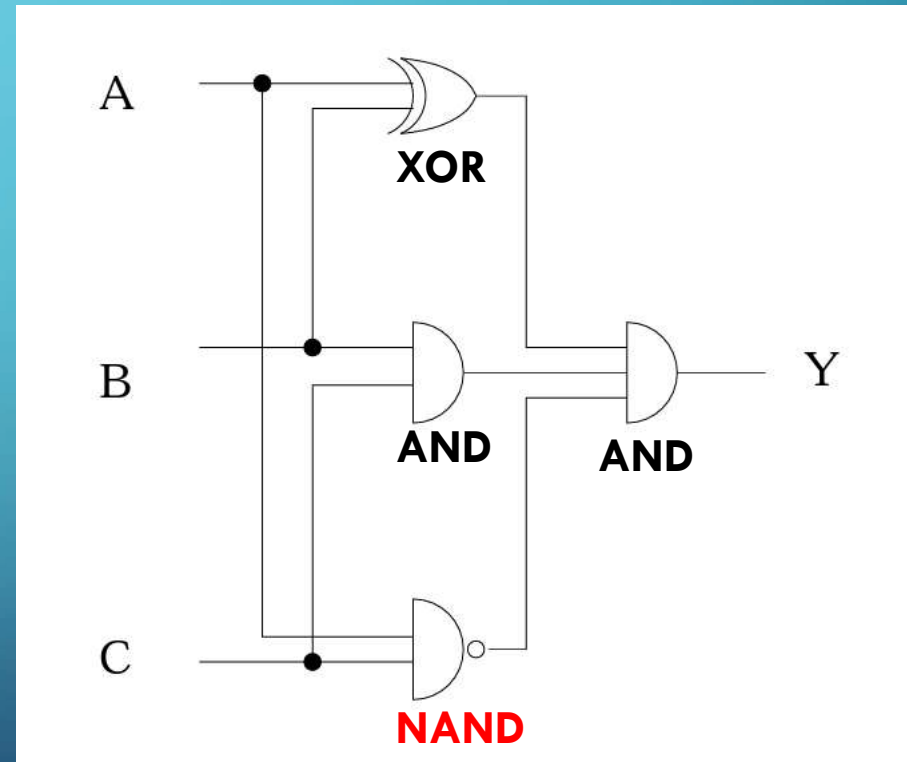
$$(A \text{ NAND } C) = (AC)' = (A'+C')$$




PROVIDE THE PRODUCT-OF-SUMS FUNCTION THAT IMPLEMENTS THE FOLLOWING COMBINATIONAL CIRCUIT

$$(A \text{ XOR } B) = A'B + AB' = (A+B)(A'+B')$$


$$(B \text{ AND } C) = BC = (B)(C)$$

$$(A \text{ NAND } C) = (AC)' = (A'+C')$$

$$Y = (A+B)(A'+B')(B)(C)(A'+C')$$

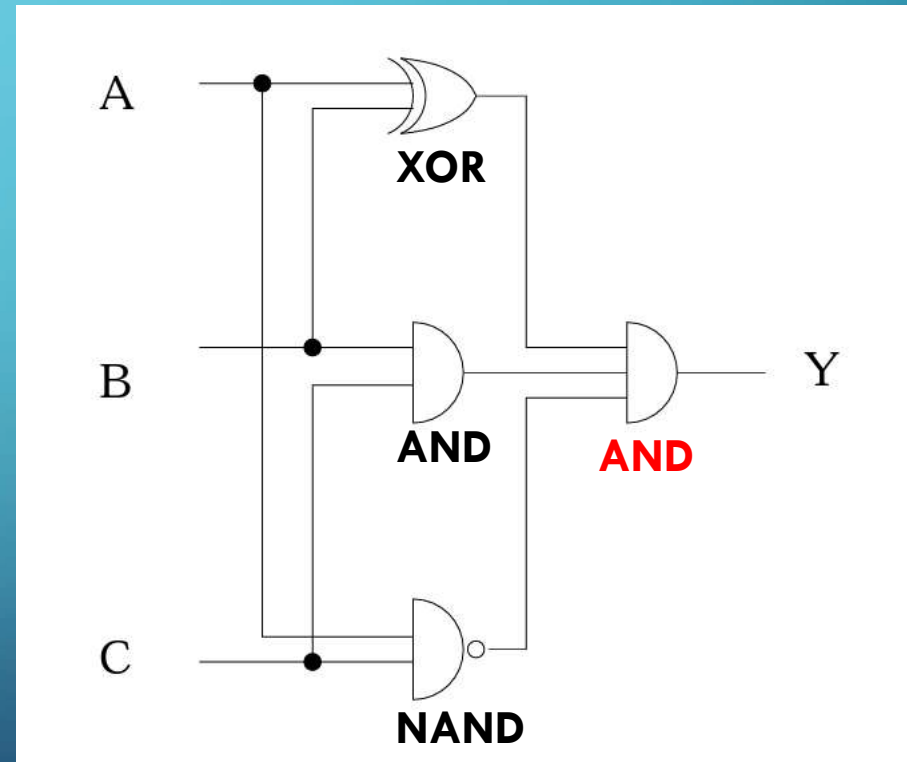


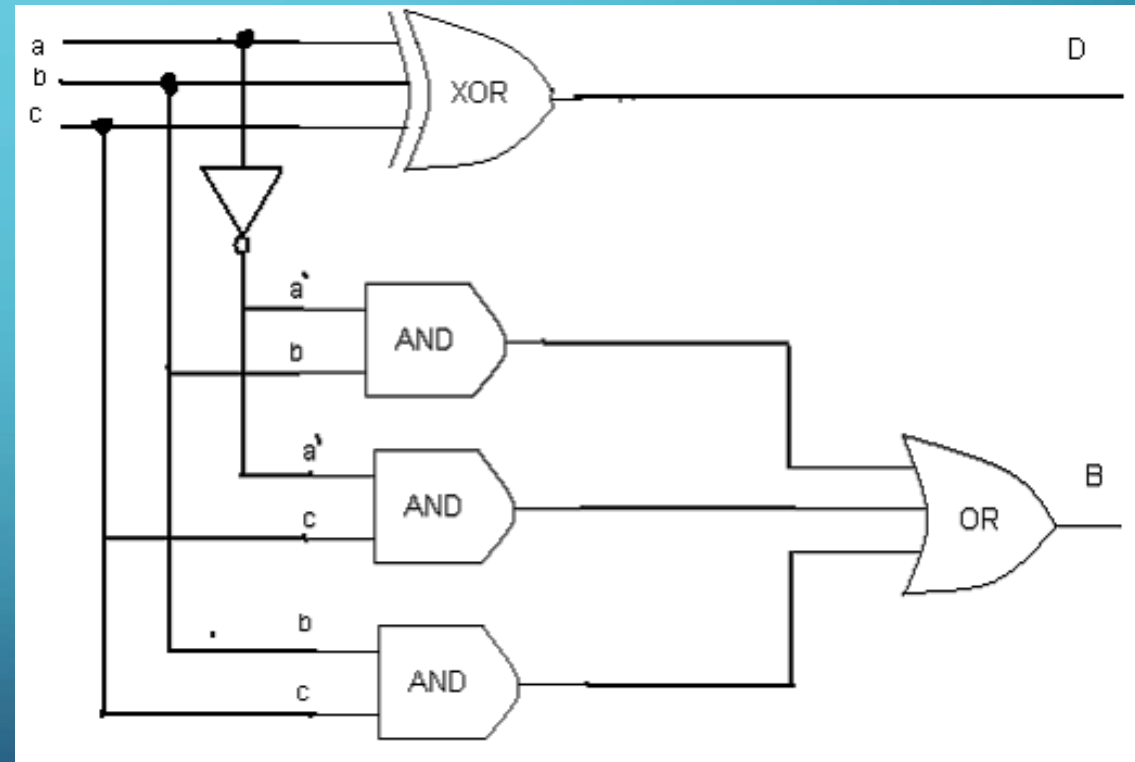WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING
COMBINATIONAL CIRCUIT IMPLEMENT?




WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

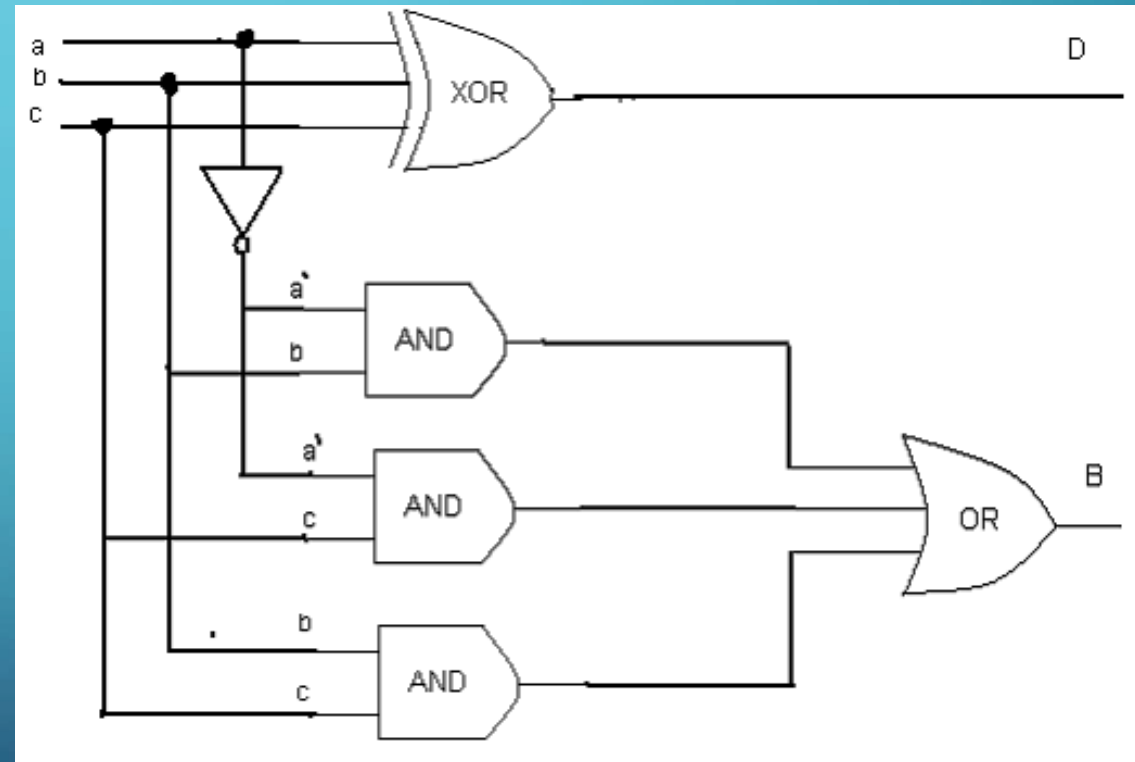


WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0	0				
0	0	1	0				
0	1	0	1				
0	1	1	1				
1	0	0	0				
1	0	1	0				
1	1	0	0				
1	1	1	0				

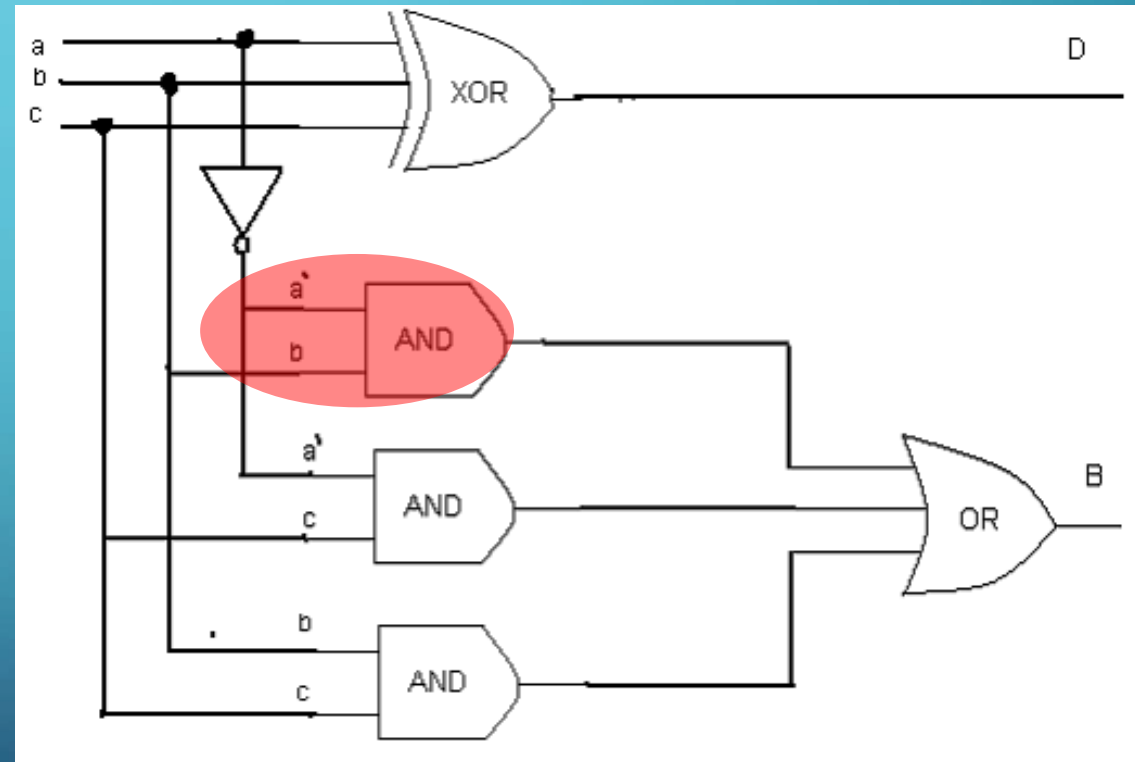


WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0	0	0			
0	0	1	0	1			
0	1	0	1	0			
0	1	1	1	1			
1	0	0	0	0			
1	0	1	0	0			
1	1	0	0	0			
1	1	1	0	0			

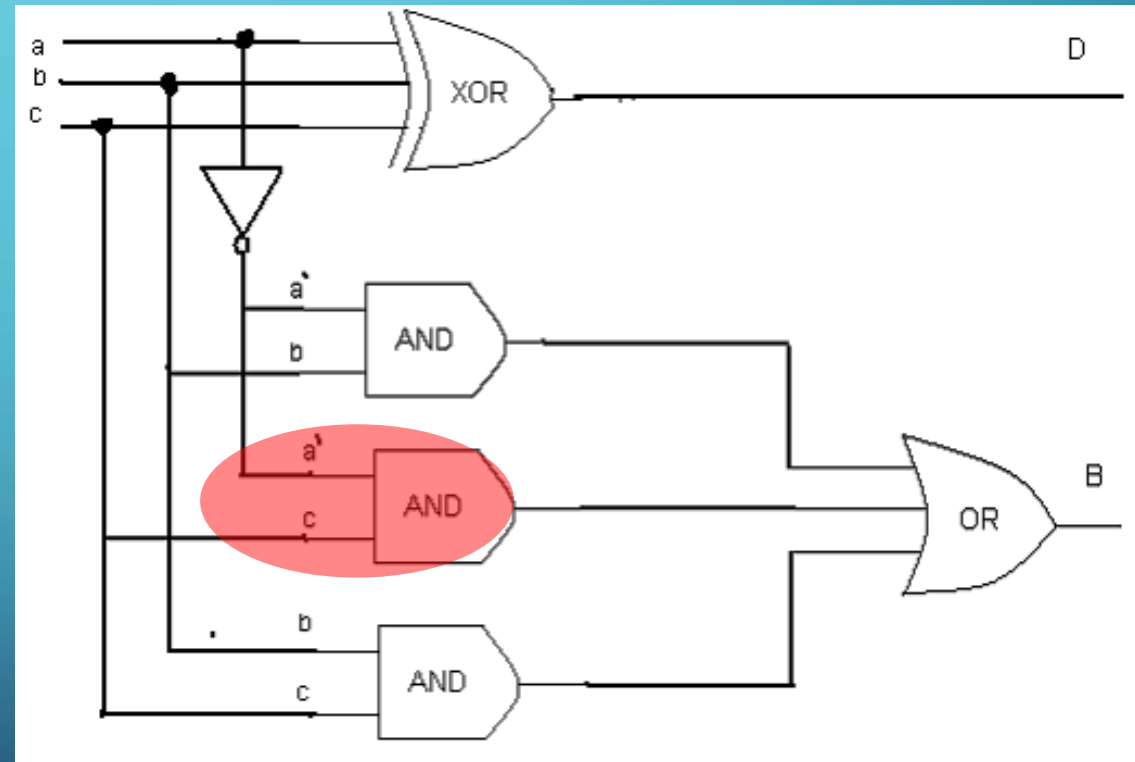


WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0	0	0	0		
0	0	1	0	1	0		
0	1	0	1	0	0		
0	1	1	1	1	1		
1	0	0	0	0	0		
1	0	1	0	0	0		
1	1	0	0	0	0		
1	1	1	0	0	1		

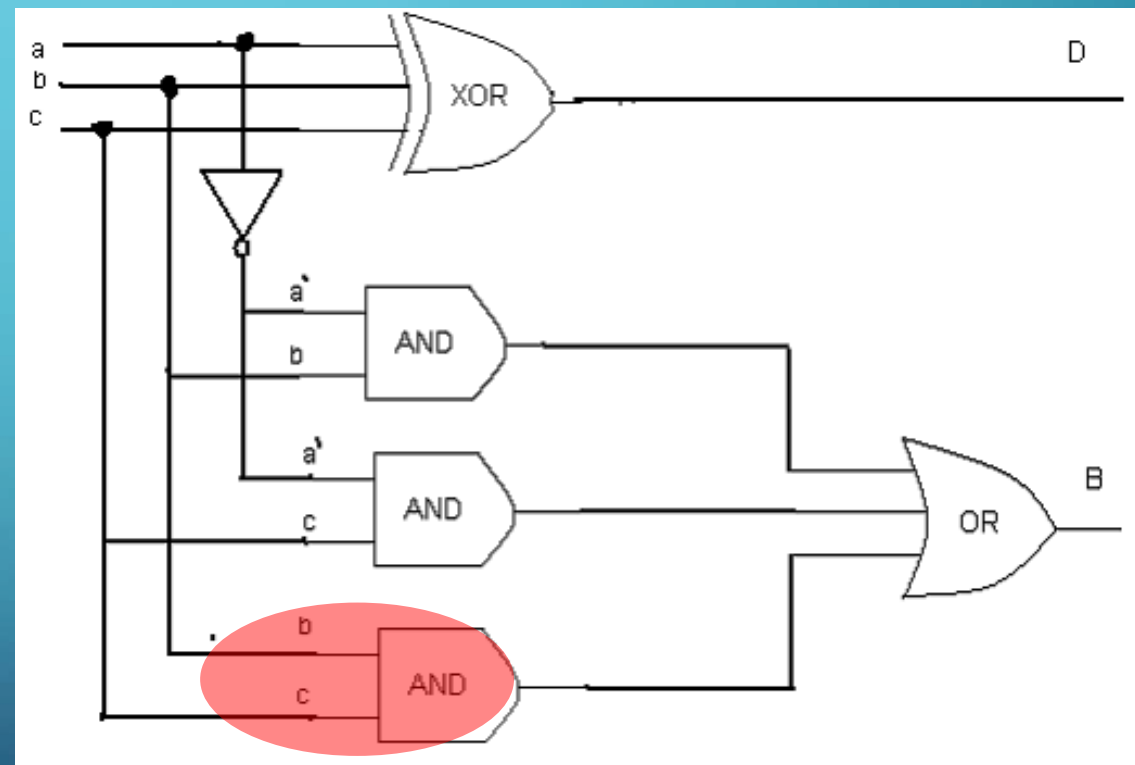


WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0	0	0	0	0	
0	0	1	0	1	0	1	
0	1	0	1	0	0	1	
0	1	1	1	1	1	0	
1	0	0	0	0	0	1	
1	0	1	0	0	0	0	
1	1	0	0	0	0	0	
1	1	1	0	0	1	1	

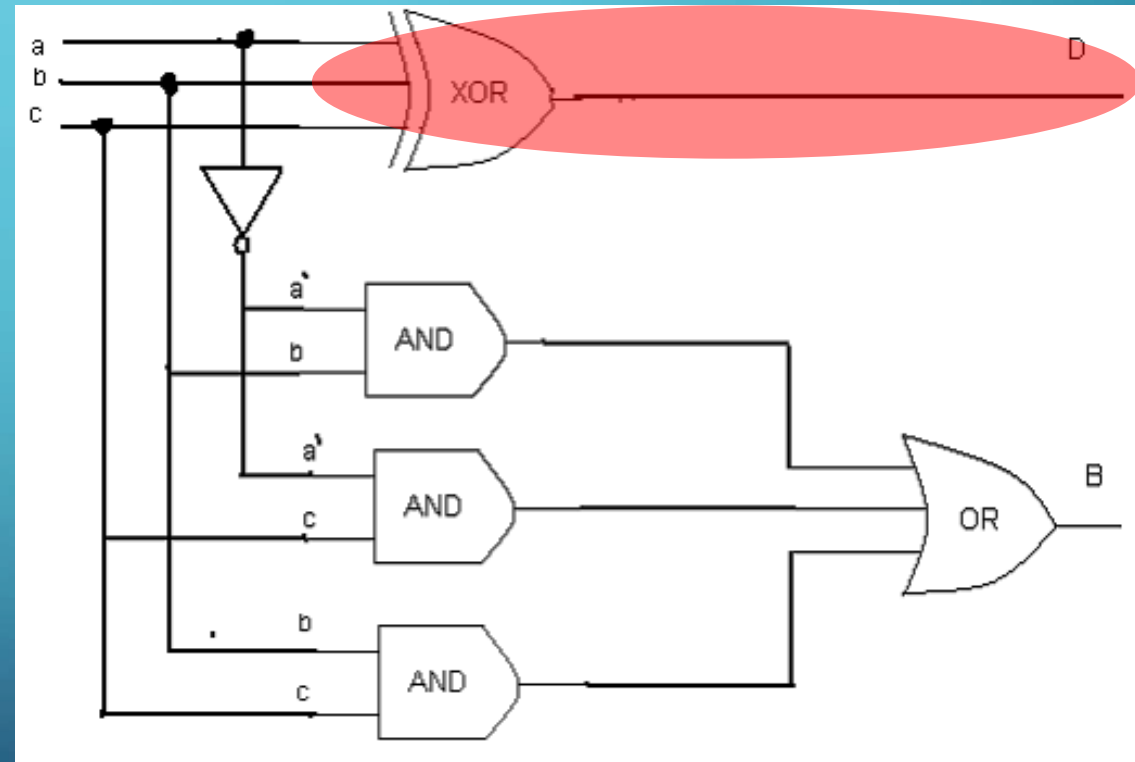


WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	$a'b$	$a'c$	bc	D	B
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	1
0	1	0	1	0	0	1	1
0	1	1	1	1	1	0	1
1	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	0	0	1	1	1

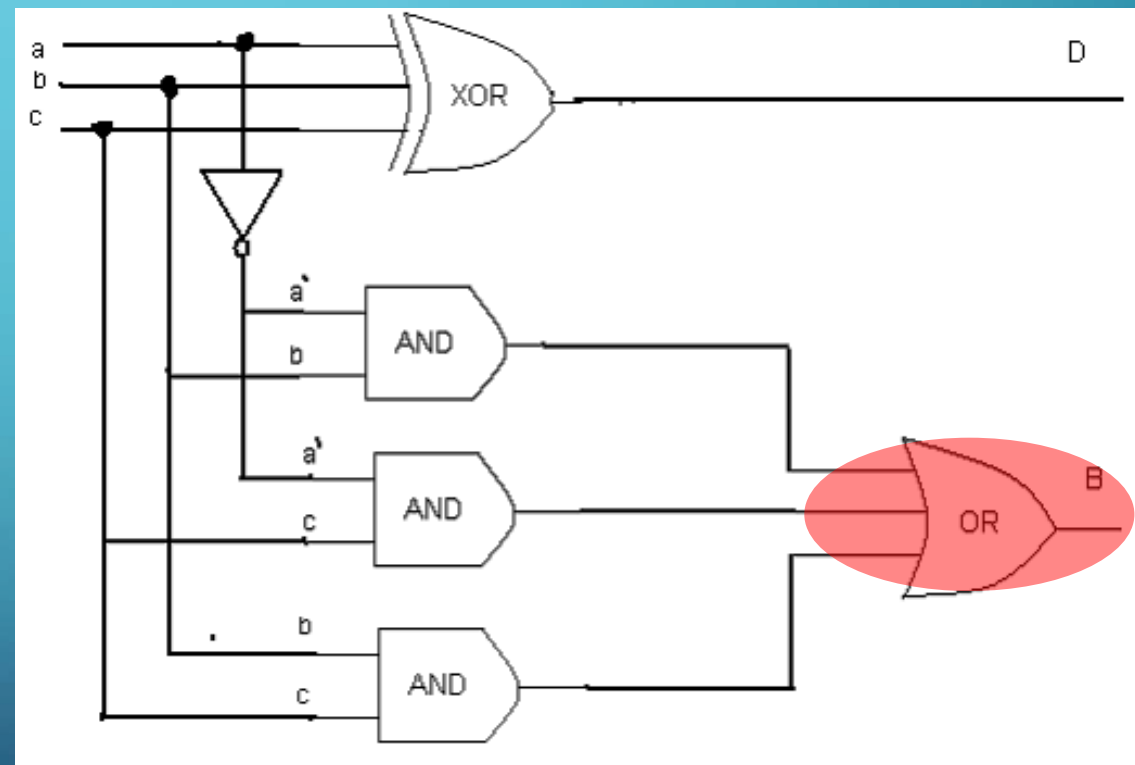

WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

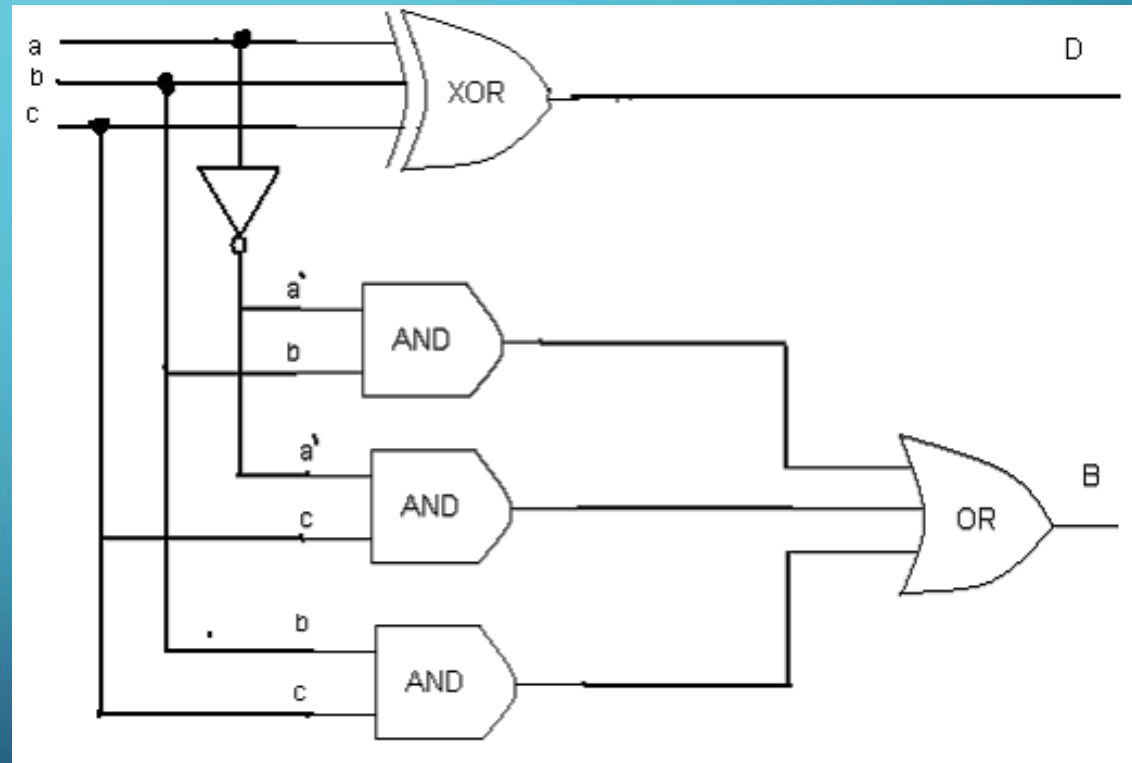

WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full subtractor:

A circuit used for the subtraction of three input bits: **minuend** a , **subtrahend** b , and **borrow in** c .

WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full subtractor:

A circuit used for the subtraction of three input bits: **minuend a** , **subtrahend b** , and **borrow in c** .

It generates two output bits: **difference D** and **borrow out B** .

WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full subtractor:

A circuit used for the subtraction of three input bits: **minuend a** , **subtrahend b** , and **borrow in c** .

It generates two output bits: **difference D** and **borrow out B** .

The borrow in c is set when the previous digit is borrowed from a . Thus, the subtrahend b and borrow in c are both subtracted from a .

WHICH ARITHMETIC FUNCTION DOES THE FOLLOWING COMBINATIONAL CIRCUIT IMPLEMENT?

a	b	c	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full subtractor:

A circuit used for the subtraction of three input bits: **minuend a** , **subtrahend b** , and **borrow in c** .

It generates two output bits: **difference D** and **borrow out B** .

The borrow in c is set when the previous digit is borrowed from a . Thus, the subtrahend b and borrow in c are both subtracted from a .

A **borrow out B** needs to be generated **when $a < b + c$** . When a borrow out is generated, 2 is added in the current digit.

Therefore, the computed difference is **$D = a - b - c + 2B$** .