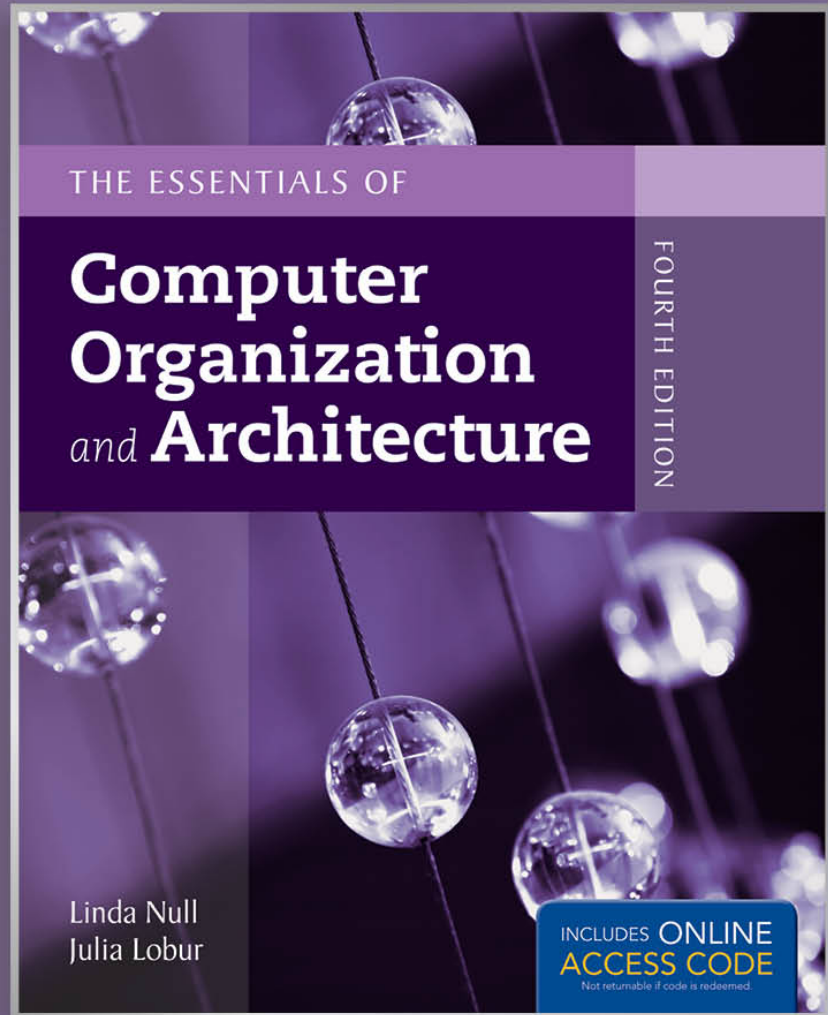


Chapter 3 Special Section

Karnaugh Maps



3A.1 Introduction

- **Simplification of Boolean functions leads to simpler and faster circuits.**
- **Simplifying functions using identity laws is time-consuming and error-prone.**
- **This section presents Karnaugh Maps (Kmaps), an easy, systematic method for reducing Boolean functions.**

3A.2 Description of Kmaps

- A Kmap is a **matrix consisting of rows and columns** that **represent the output values** of a **Boolean function**.
- The **output values** placed in each cell are **derived from the minterms** of a function.
- A **minterm** is a **Boolean product** that contains **all variables exactly once**, either **complemented or not complemented**.

3A.2 Description of Kmaps

- The minterms for a function having the inputs x and y are $x'y'$, $x'y$, xy' , and xy .
- Consider the Boolean function, $F(x, y) = xy + xy'$
- **Minterm table:**

Minterm	X	Y
$x'y'$	0	0
$x'y$	0	1
xy'	1	0
xy	1	1

3A.2 Description of Kmaps

- Minterm table of a function with variables x, y, z:

Minterm	X	Y	Z
$X'Y'Z'$	0	0	0
$X'Y'Z$	0	0	1
$X'YZ'$	0	1	0
$X'YZ$	0	1	1
$XY'Z'$	1	0	0
$XY'Z$	1	0	1
XYZ'	1	1	0
XYZ	1	1	1

3A.2 Deriving Kmaps from Truth Tables

$$F(x, y) = (x' y) + (x y') + (x y)$$

X	Y	$F(x, y)$
0	0	0
0	1	1
1	0	1
1	1	1

3A.2 Deriving Kmaps from Truth Tables

$$F(x, y, z) = (x'yz') + (x'yz) + (xy'z') + (xyz') + (xyz)$$

x	y	z	F (x , y , z)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

3A.2 Description of Kmaps

- A Kmap has a **cell for each minterm**.
- This means that it has a **cell for each line of the truth table** of a function.
- **Example:**

$$F(X, Y) = XY$$

X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X \ Y	0	1
	0	1
0	0	0
1	0	1

3A.3 Kmap Simplification for Two Variables

- We can **reduce the function** of the Kmap to its simplest terms **by finding neighbored 1s** that can be collected into groups **that are powers of two**.
- Possible group sizes are 1, 2, 4, 8, 16, ...

- In our example, we have two such groups.
 - Can you find them?

x \ y	0	1
0	0	1
1	1	1

3A.3 Kmap Simplification for Two Variables

- We see that **both groups are powers of two** and that the **groups overlap**.
- The next slide gives guidance for selecting Kmap groups.

X \ Y	0	1
0	0	1
1	1	1

3A.3 Kmap Simplification for Two Variables

The **rules** of Kmap simplification are:

- Groups can contain **1s only**; no 0s.
- Groups can be formed only at **right angles**; diagonal groups are not allowed.
- The **group sizes** must be a **power of 2** – even if it contains a single 1.
- The **groups must** be made **as large as possible**.
- **Groups can overlap** and **wrap around** the sides of the Kmap.

3A.3 Kmap Simplification for Three Variables

$$F(X, Y, Z) = X'Y'Z + X'YZ + XY'Z + XYZ$$

- What is the largest group of 1s that is a power of 2?

X \ YZ	YZ			
	00	01	11	10
0	0	1	1	0
1	0	1	1	0

3A.3 Kmap Simplification for Three Variables

- This group tells us that changes in the variables x and y have no influence on the value of the function: They are irrelevant.
- This means that the function,

$$F(X, Y, Z) = X'Y'Z + X'YZ + XY'Z + XYZ$$

reduces to $F(z) = z$.

x \ yz	yz			
	00	01	11	10
0	0	1	1	0
1	0	1	1	0

3A.3 Kmap Simplification for Three Variables

- A more complicated Kmap:

$$F(X, Y, Z) = X'Y'Z' + X'Y'Z + X'YZ + X'YZ' + XY'Z' + XYZ'$$

- Its Kmap is shown below. There are (only) two groupings of 1s.
 - Can you find them?

x \ yz	yz			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

3A.3 Kmap Simplification for Three Variables

- The **pink group wraps around** the sides of a Kmap.
- This group tells us that the **values of x and y are not relevant** to the term of the function that is represented by the group.
- The **reduced term** of this group is z'

What about the green group in the top row?

X \ YZ	YZ			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

3A.3 Kmap Simplification for Three Variables

- The **green group** tells us that **only the value of x is relevant** in that group.
- **x** is complemented in that row, so the **reduced term** of corresponding to this group is **X'** .
- The reduced function the sum of terms of all groups:
$$F(X, Z) = X' + Z'$$

Recall that we had
six minterms in our
original function!

X \ YZ	YZ			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

3A.3 Kmap Simplification for Four Variables

- General format of a **Kmap** of a function with **4 variables** and **16 minterms**:

wx \ yz	yz			
	00	01	11	10
00	$w'x'y'z'$	$w'x'y'z$	$w'x y z$	$w'x'y z'$
01	$w'x y'z'$	$w'x y'z$	$w'x y z$	$w'x y z'$
11	$w x'y'z'$	$w x'y'z$	$w x y z$	$w x'y z'$
10	$w x y'z'$	$w x y'z$	$w x y z$	$w x y z'$

3A.3 Kmap Simplification for Four Variables

- Example (only non-zero minterms shown):

$$F(W, X, Y, Z) = W'X'Y'Z' + W'X'Y'Z + W'X'YZ' + W'XYZ' + WX'Y'Z' + WX'Y'Z + WX'YZ'$$

- Can you identify (only) three groups in this Kmap?


Recall that groups can overlap and wrap around.

WX \ YZ	YZ			
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

3A.3 Kmap Simplification for Four Variables

- The three groups consist of:
 - A **purple group** entirely within the Kmap at the right.
 - A **pink group** that wraps the top and bottom.
 - A **green group** that spans the corners.
- We have three terms in our final function:

$$F(W, X, Y, Z) = X'Y' + X'Z' + W'YZ'$$

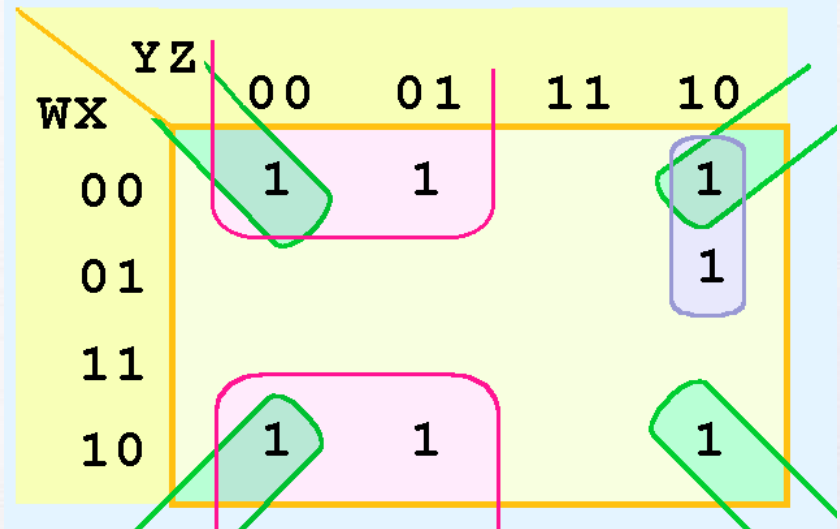

3A.3 Kmap Simplification for Four Variables

- It is **possible to have a choice** as to how to pick groups within a Kmap, while keeping the groups as large as possible.
- The **different functions** that result from the groupings below are **logically equivalent**.

WX \ YZ	YZ			
	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

WX \ YZ	YZ			
	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

3A.6 Don't Care Conditions

- Consider the function $F(w,x,y,z)$ that returns whether the **quotient wx/yz has a remainder**
- Examples:
 - $01_2/10_2 = 1/2$ has a remainder, output: 1
 - $11_2/11_2 = 3/3$ has no remainder, output: 0
 - $10_2/00_2 = 2/0$ is an **invalid input**, output: undefined
- Circuits must be designed such that **invalid inputs will never happen**
- In a Kmap, we **don't need to care** whether the output corresponding to an invalid input is 0 or 1

3A.6 Don't Care Conditions

- Consider the function $F(w,x,y,z)$ that returns whether the **quotient wx/yz has a remainder**

WX \ YZ	YZ			
	00	01	11	10
00	X			
01	X		1	1
11	X			1
10	X		1	

- The **cross X** indicates ‘**don’t care**’ cases (division by 0)
- When building groups, we are **free to include or ignore the X ’s**

3A.6 Don't Care Conditions

- Consider the function $F(w,x,y,z)$ that returns whether the **quotient wx/yz has a remainder**

WX \ YZ	YZ			
	00	01	11	10
00	X			
01	X		1	1
11	X			1
10	X		1	

- Simplified function $F(w,x,y,z) = xz' + w'xy + wx'yz$
- We included **some** X's in order to get larger groups

3A.6 Don't Care Conditions

- Second example:

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

3A.6 Don't Care Conditions

- One possible solution:

$$F(W, X, Y, Z) = W'X' + YZ$$

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

3A.6 Don't Care Conditions

- Another possible solution:

$$F(W, X, Y, Z) = W'Z + YZ$$

WX \ YZ	YZ			
	00	01	11	10
00	×	1	1	×
01		×	1	
11	×		1	
10			1	

3A.6 Don't Care Conditions

- The truth table of: $F(W, X, Y, Z) = W' X' + YZ$

differs from the truth table of:

$$F(W, X, Y, Z) = W' Z + YZ$$

- However, the values for which they differ, are the inputs for which we have **don't care** conditions.

WX \ YZ	YZ			
	00	01	11	10
00	×	1	1	×
01		×	1	
11	×		1	
10			1	

WX \ YZ	YZ			
	00	01	11	10
00	×	1	1	×
01		×	1	
11	×		1	
10			1	

3A Summary

- **Kmaps** provide an easy graphical method for **simplifying Boolean functions**.
- A Kmap is a **matrix** consisting **of the outputs** of the minterms of a Boolean function.
- In this section, we have discussed 2- 3- and 4-input Kmaps. This method **can be extended to any number** of inputs through the use of multiple tables.

3A Summary

Recapping the **rules of Kmap simplification**:

- Groupings can contain only 1s; no 0s.
- Groups can be formed only at right angles; diagonal groups are not allowed.
- The number of 1s in a group must be a power of 2 – even if it contains a single 1.
- The groups must be made as large as possible.
- Groups can overlap and wrap around the sides of the Kmap.
- Use don't care conditions when you can.

3A Exercise

- Build a Kmap corresponding to the following truth table
- Derive the simplified function via building groups

A	B	C	D	Out
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1